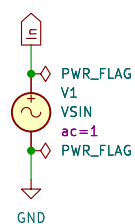
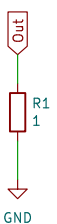




; f0 = 1/(2*pi*sqrt(LC)) = 159 155 Hz
; At f0, impedance is LOW and current HIGH



.ac dec 1000 1 10meg

GitHub/OJStuff		
Sheet: /		
File: LC-Series-resonance-(.ac).kicad_sch		
Title: LC Series resonance		
Size: A4	Date: 2024-02-27	Rev: 1
KiCad E.D.A. kicad 7.0.10		Id: 1/1